

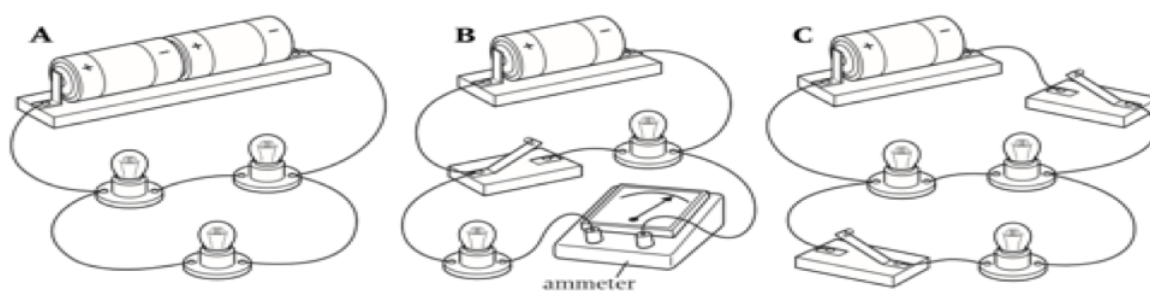
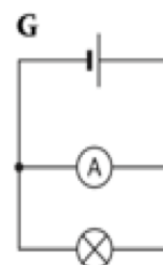
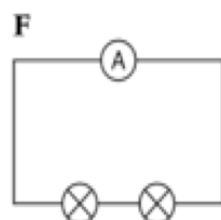


Drawing circuit diagrams

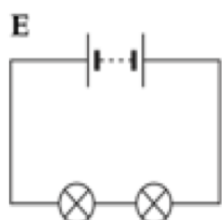- ① Draw circuit diagrams using the correct symbols for the following circuits



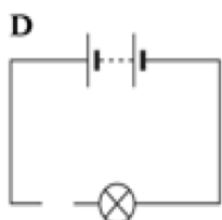- ② John drew circuit diagrams for homework but made a mistake in each diagram. Identify the mistake and draw the correct version.



- ③ Which circuit is the odd one out? Explain your answer.

